



Department of Computer Science and Engineering

Course Title: Electrical Circuits

Course Number: 209

Semester: 4th

Experiment No.: 07

Experiment Title: DC Circuit Analysis in PSpice using source and Resistance Sweep.

Student ID: 2020-3-60-012

Student Name: Sadia Islam Prova

Date of Performance: 23-12-21

Date of Report Submission: 07-01-22

Objectives:

1. To analyze DC circuit in PSpice by sweeping source and resistance.
2. To verify maximum power transfer theorem.

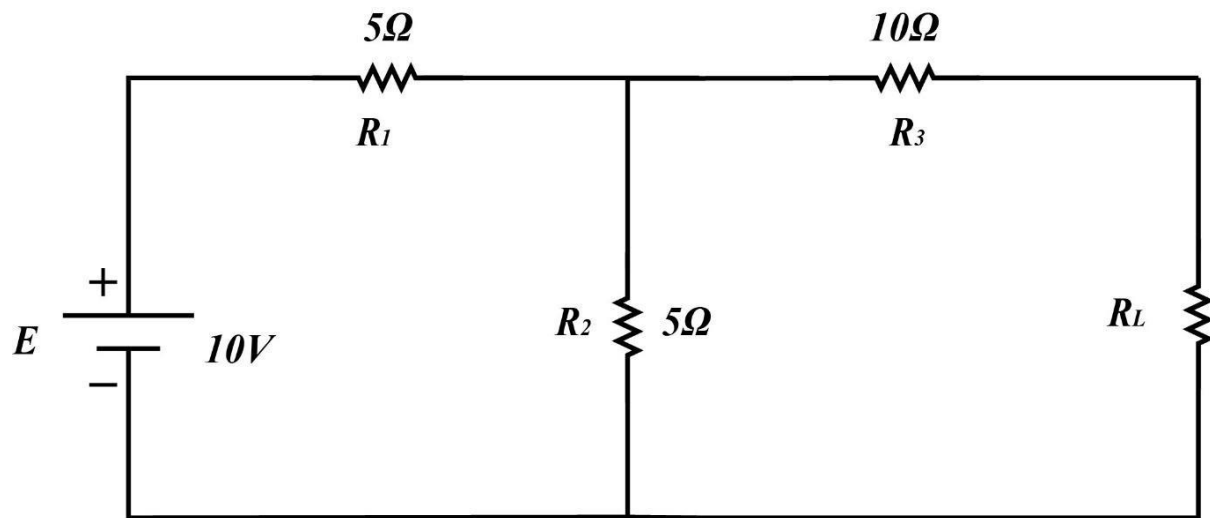
Circuit Diagram:

Figure 1: Circuit diagram for experiment

Answer to the post lab report question 01:


From PSpice generated graph we identified,

$$V(1) = 4.44 \text{ V}$$

$$V(2) = 2.22 \text{ V}$$

$$I(R_3) = 222.22 \text{ mA}$$

These values are same for the step 4 and step 5(d).

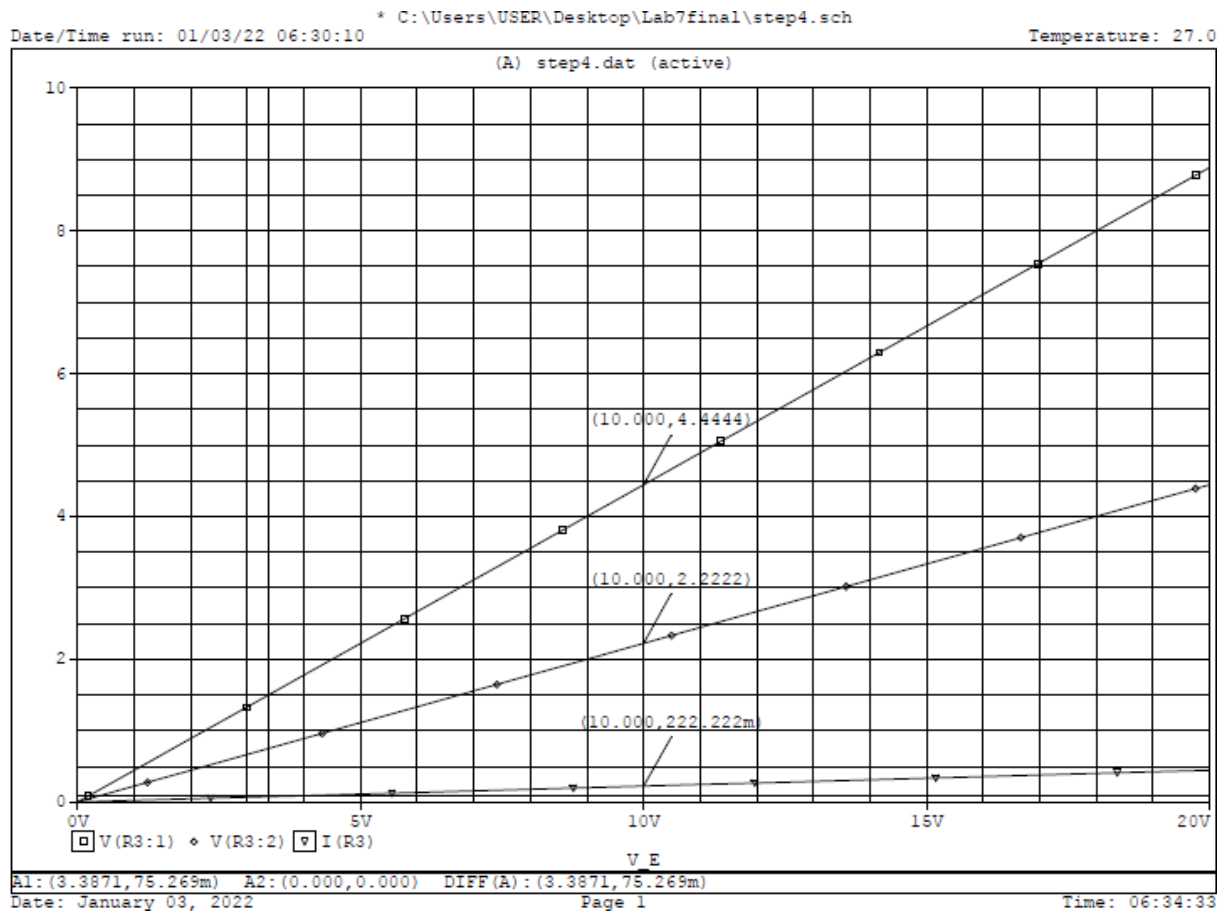**Figure 2: graph for step 4**

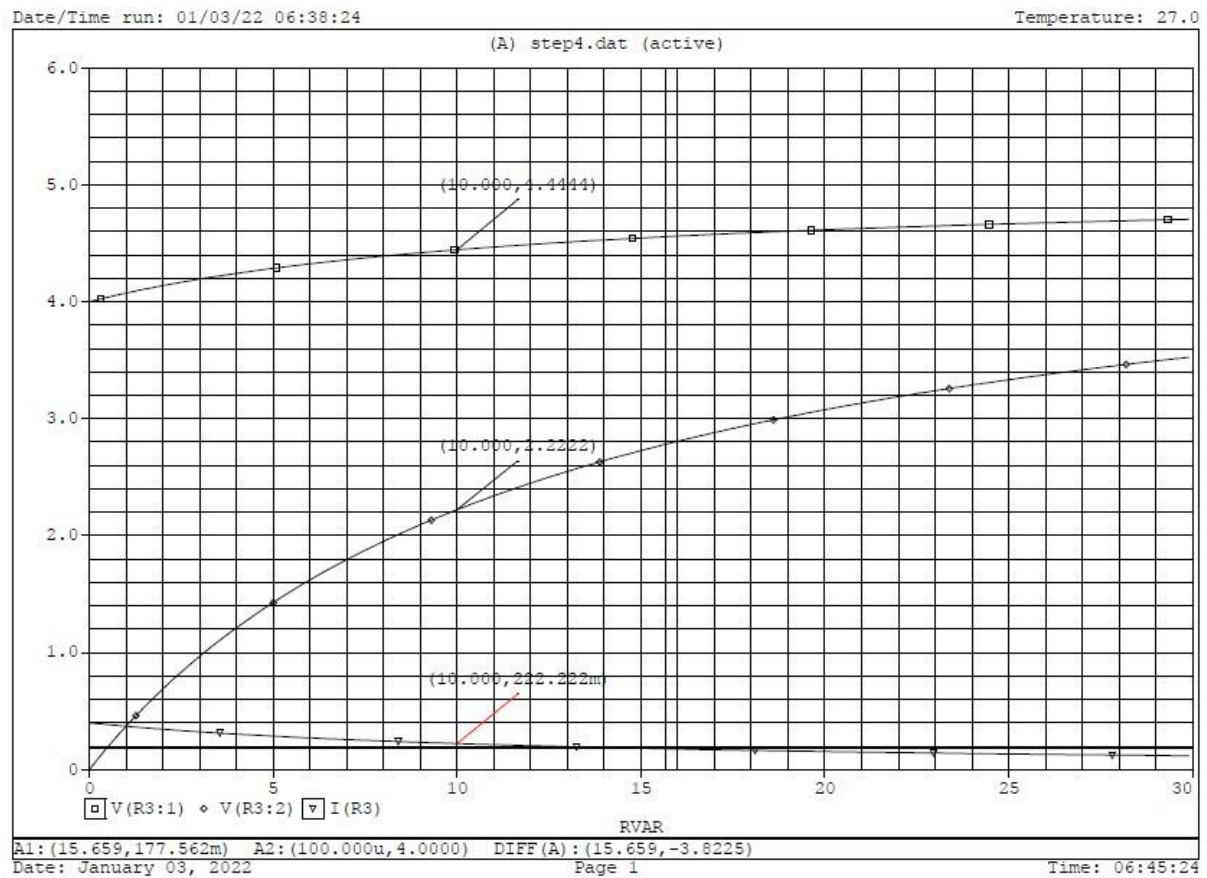


Figure 3: graph for step 5.d

Answer to the post lab report question 02:

From PSpice step 3 simulation we have

(step 3) $VOC = 5\text{ V}$

$ISC = 0.4\text{ A}$

$$\therefore R_{th} = (5/0.4 \text{ } \Omega) = 12.5 \text{ } \Omega$$

From step 5(e) PSpice generated graph we have

Maximum power at load resistant 12.5Ω

$$\therefore R_{th} = R_L = 12.5 \text{ } \Omega$$

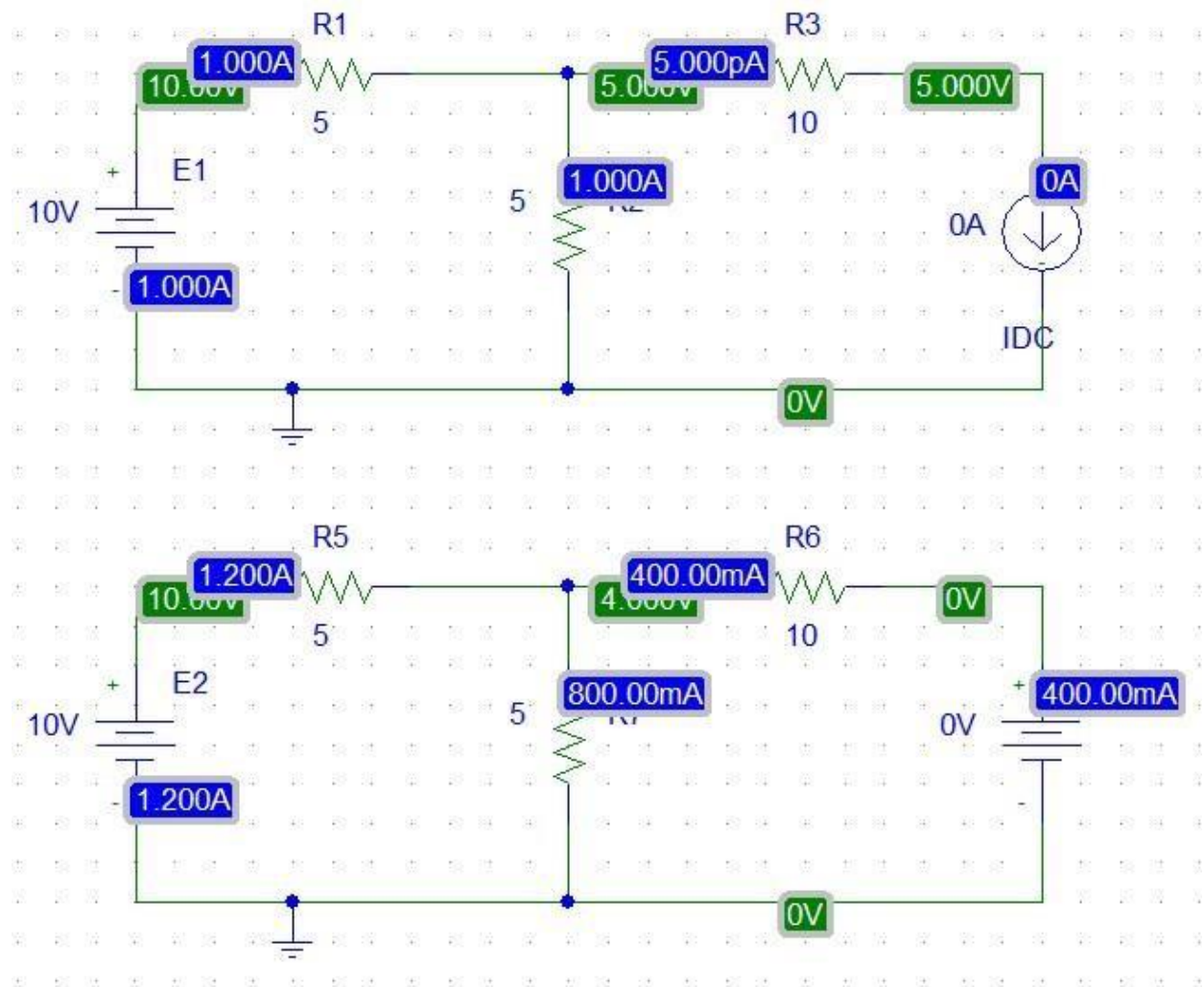


Figure 4: Circuit simulation in PSpice



After comparing the values there is no discrepancy in PSpice.

Conclusion:

In this experiment we verified the maximum power theorem and analyzed DC circuit in PSpice and found no discrepancy with our actual value in PSpice.

