



Department of Computer Science and Engineering

Course Title: Electrical Circuits

Course Number: 209

Semester: 4th

Experiment No.: 01

Experiment Title: Introduction to Circuit Elements and Variables

Student ID: 2020-3-60-012

Student Name: Sadia Islam Prova

Date of Performance: 20-11-21

Date of Report Submission: 07-01-2022

Objectives of the Experiment:

1. To get familiar with circuit variables (voltage and current) and circuit elements (voltage source and resistance).
2. To learn how to measure dc voltage across a circuit element using a voltmeter.
3. To learn how to measure dc current through a circuit element using an ammeter.
4. To learn how to measure resistance of a resistor using a multimeter.
5. To verify Ohm's Law.

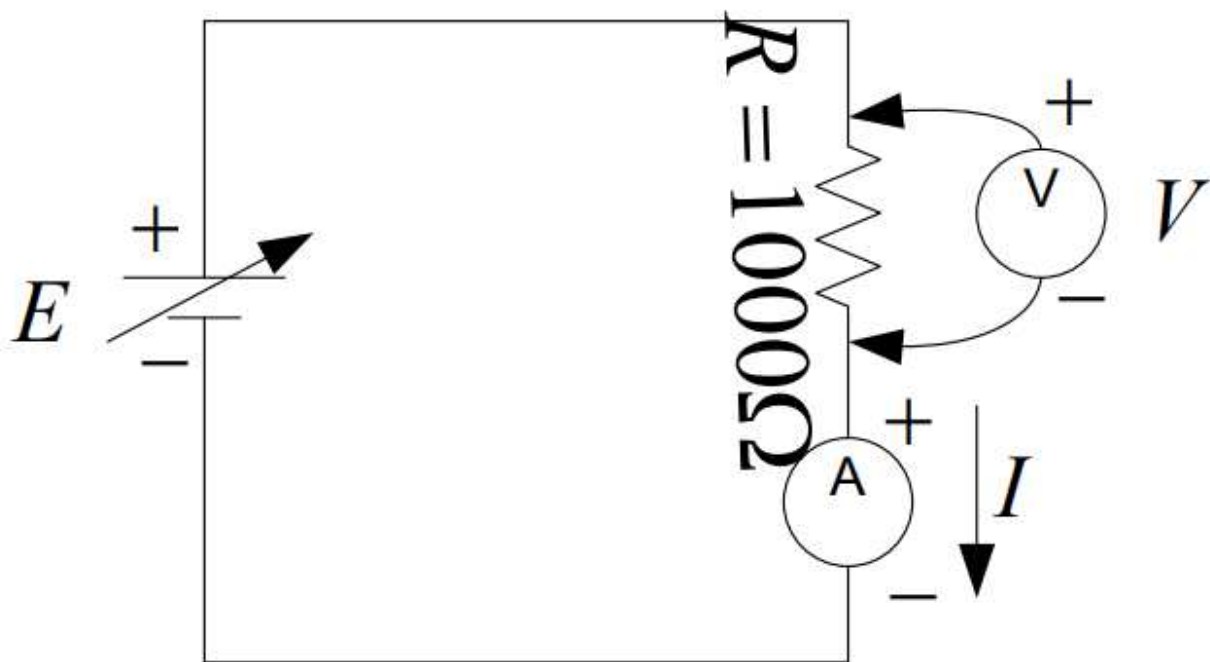
Circuit Diagram:

Figure: Circuit for Experiment

Table 01 .Experimental Datasheet:

Observation Number	Set value of E (V)	Measured value Of V (V)	Measured value Of I (mA)	Measured value of R ((Ω))
1	5	5	5	1000
2	6	6	6	
3	7	7	7	
4	8	8	8	
5	9	9	9	
6	10	10	10	

Answers to the post lab report questions:01

$$1. I = \frac{V}{R} = \frac{5}{1000} \text{ mA} = 5 \text{ mA}$$

$$2. I = \frac{V}{R} = \frac{6}{1000} \text{ mA} = 6 \text{ mA}$$

$$3. I = \frac{V}{R} = \frac{7}{1000} \text{ mA} = 7 \text{ mA}$$

$$4. I = \frac{V}{R} = \frac{8}{1000} \text{ mA} = 8 \text{ mA}$$

$$5. I = \frac{V}{R} = \frac{9}{1000} \text{ mA} = 9 \text{ mA}$$

$$6. I = \frac{V}{R} = \frac{10}{1000} \text{ mA} = 10 \text{ mA}$$

There is no discrepancy in PSpice.

Answers to the post lab report questions:02

$$1. R = \frac{V}{I} = \frac{5V}{5 \text{ mA}} = 1000 \, \Omega$$

$$2. R = \frac{V}{I} = \frac{6V}{6 \text{ mA}} = 1000 \, \Omega$$

$$3. R = \frac{V}{I} = \frac{7V}{7 \text{ mA}} = 1000 \, \Omega$$

$$4. R = \frac{V}{I} = \frac{8V}{8 \text{ mA}} = 1000 \, \Omega$$


$$5. R = \frac{V}{I} = \frac{9V}{9 \text{ mA}} = 1000 \, \Omega$$

$$6. R = \frac{V}{I} = \frac{10V}{10 \text{ mA}} = 1000 \, \Omega$$

There is no discrepancy in PSpice.

Answers to the post lab report questions:03

There is no discrepancy in PSpice and the set of value of E and the measured value of V is the same.

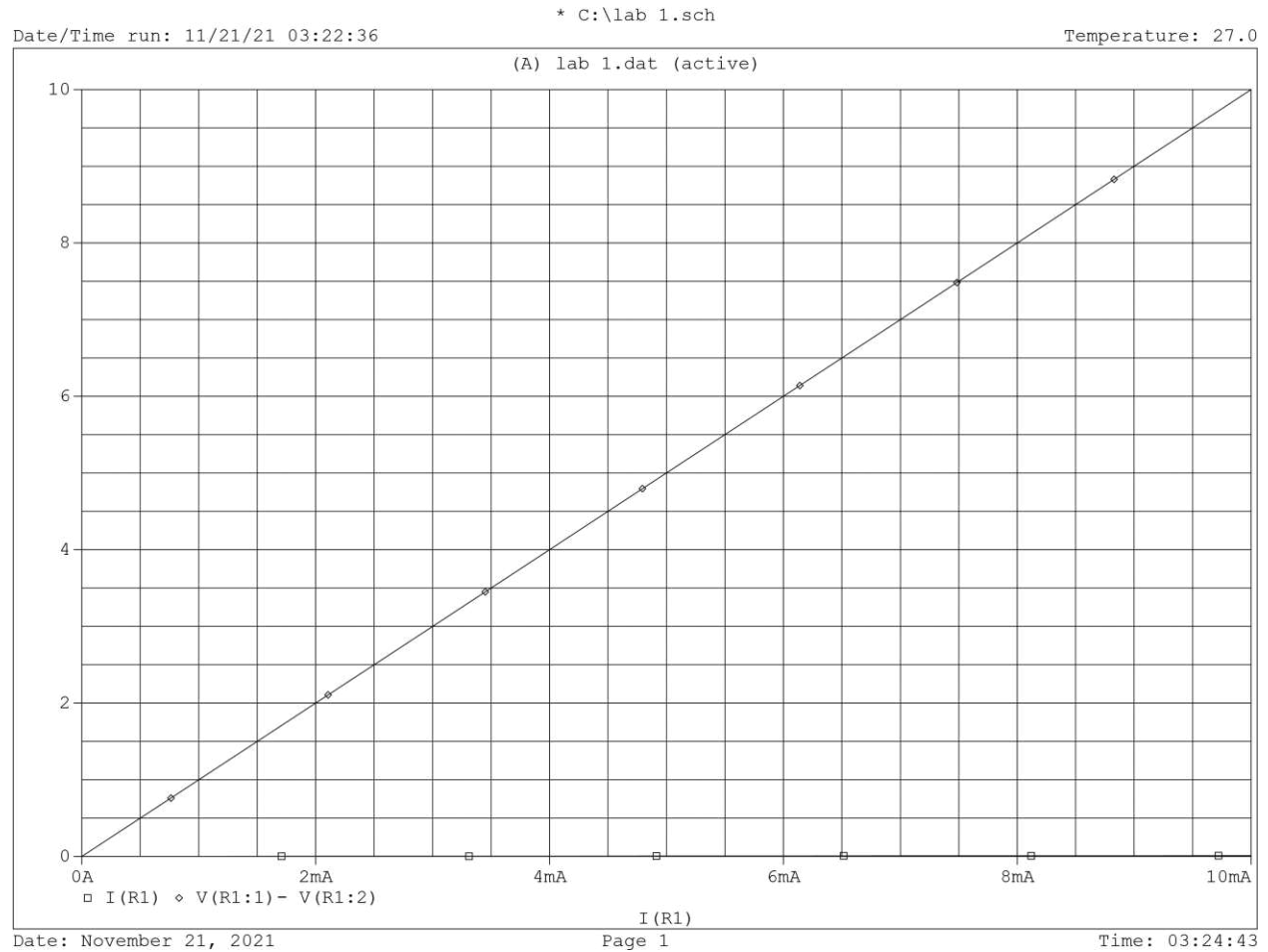Answers to the post lab report questions:04**Figure: Graph for step 4**

We know from ohm's law, $R = \frac{V}{I}$ and for graph $m = \frac{y}{x}$ the resistance ,

$$m = \frac{y}{x} = \frac{5V}{5mA} = 1000 \text{ ohm.}$$

There is no discrepancy in PSpice.

Answers to the post lab report questions:05

A multimeter can be used as ammeter, voltmeter and ohmmeter. For measuring voltage , we use voltmeter in parallel connection and for measuring current , we use ammeter in series connection. For measuring voltage and current there will be a knob which we need to put in the range.

Conclusion:

We got familiar with circuit variables (voltage and current) and circuit element (voltage source and resistance) and verified ohm's law and found no discrepancy in PSpice.