

## Experiment No: 6

Title: Verification of Thevenin's theorem

Circuit Diagrams:

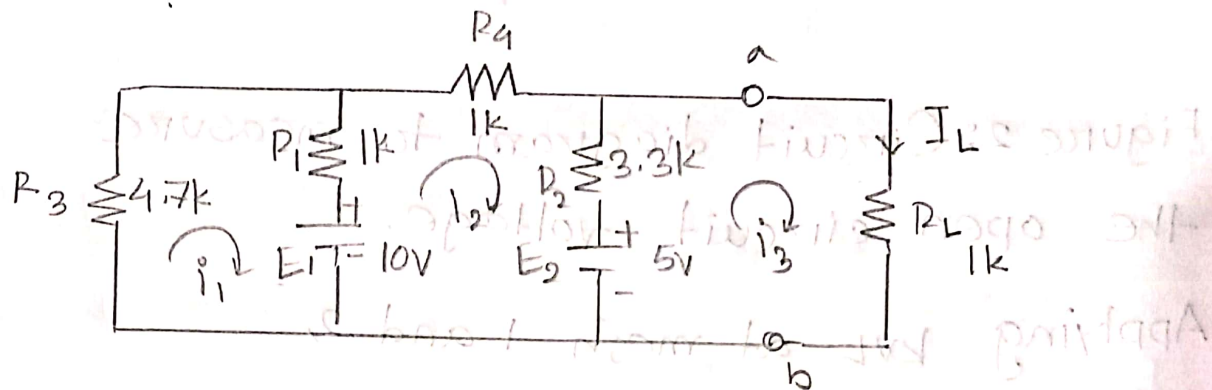


Figure: 1. Circuit diagram whose Thevenin's equivalent to be determined

$$I_L = i_3$$

Applying KVL at mesh 1, 2 and 3 respectively,

$$(5.7k)i_1 - (1k)i_2 = -10$$

$$-(1k)i_1 + (5.3k)i_2 - (3.3k)i_3 = 10 - 5$$

$$-(3.3k)i_2 + (4.3k)i_3 = 5$$

From these equations, we found,

$$i_3 = 3.26 \text{ mA}$$

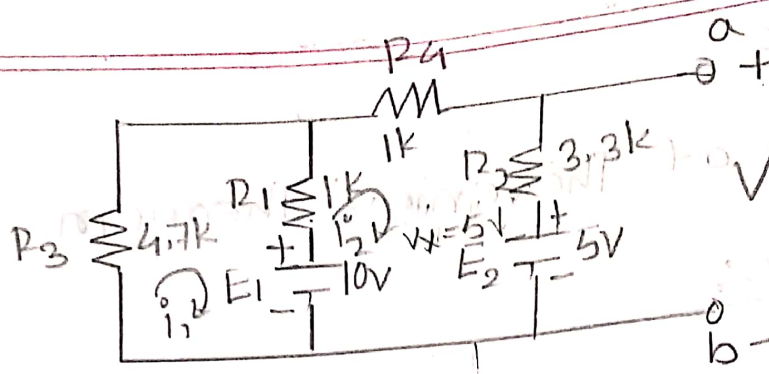


Figure 2: Circuit diagram to measure the open circuit voltage.

Applying KVL at mesh 1 and 2,

$$(5.7k)i_1 - (1k)i_2 = -10$$

$$- (1k)i_1 + (5.3k)i_2 = 5$$

Solving these, we got,

$$i_2 = 0.633 \text{ mA}$$

$$E_{Th} = 3.3k i_2 + 5 = 7.089 \text{ V}$$

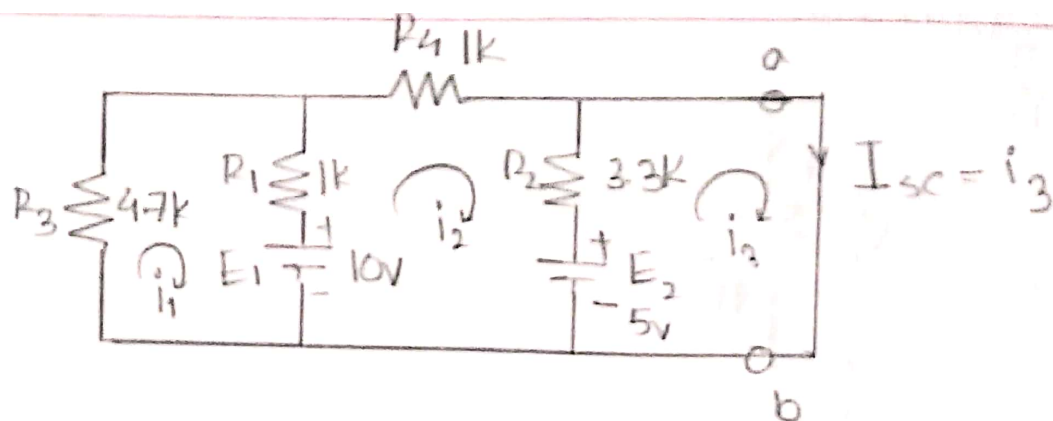


Figure 3. Circuit diagram to measure the short circuit current.

Applying KVL at mesh 1, 2, 3 respectively,

$$(5.7k) i_1 - (1k) i_2 = -10$$

$$(-1k) i_1 + (5.3k) i_2 - (3.3k) i_3 = 10 - 5$$

$$- (3.3k) i_2 + (3.3k) i_3 = 5$$

Solving these equations, we get,

$$i_3 = 6.034 \text{ mA}$$

$$R_{Th} = \frac{V_{oc}}{I_{sc}} = \frac{7.089}{6.034 \text{ mA}} = 1174.843 \Omega = 1.175 \text{ k}\Omega$$



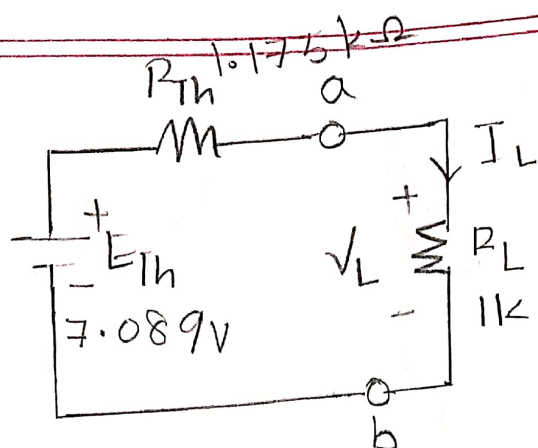


Figure 4. Circuit diagram to verify Thevenin's theorem.

$$I_L = \frac{7.089}{2.175k} \quad A = 0.00325 \text{ A} = 3.25 \text{ mA}$$