



Department of Computer Science and Engineering

Course Title: Electrical Circuits

Course Number: 209

Semester: 4th

Experiment No.: 04

Experiment Title: Bias Point Detail Analysis of DC Circuit with Dependent Sources Using PSpice Schematics.

Student ID: 2020-3-60-012

Student Name: Sadia Islam Prova

Date of Performance: 23-11-21

Date of Report Submission: 07-01-2022

Objectives:

1. To analyze Bias Point Detail of DC Circuit with Dependent Source using PSpice Schematics.

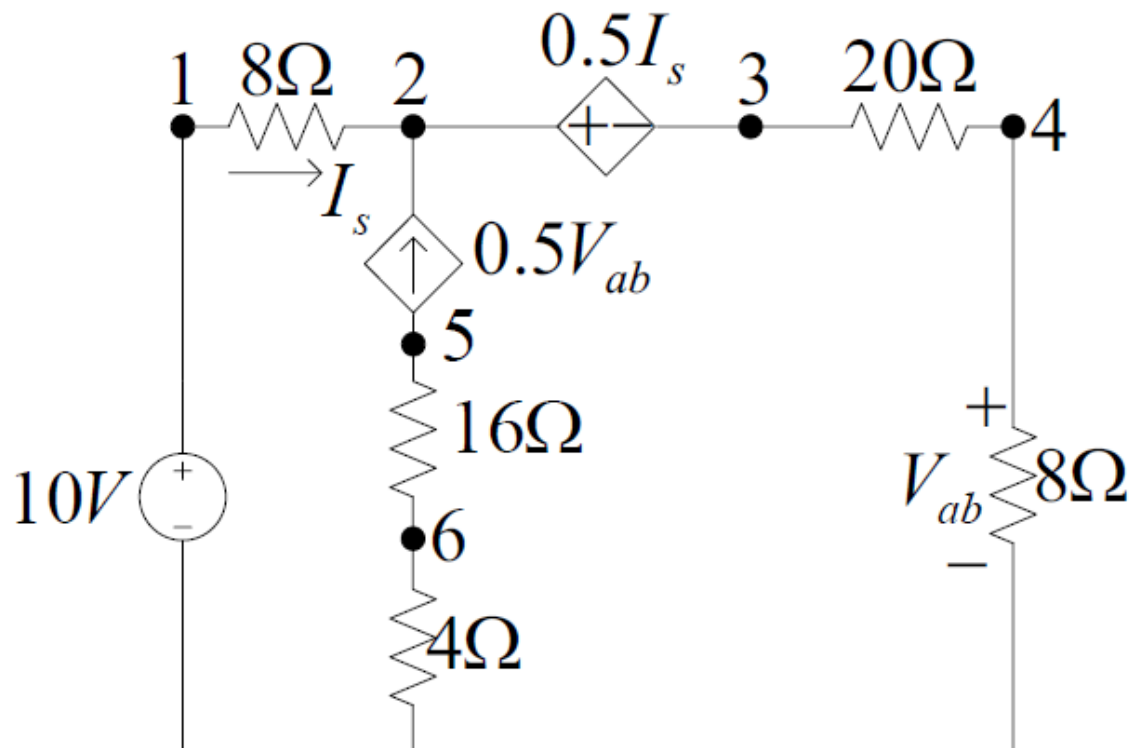
Circuit Diagram:

Figure: A circuit with VCCS and CCVS

Answer to the question of post lab report 01:

Applying KCL at node 2,

$$i_2 - i_1 = 0.5V_{ab}$$

$$\text{Or, } i_2 - i_1 = 4i_2 \dots\dots\dots (1)$$

Applying KVL at SM1,

$$10 - 8i_1 - 0.5I_s - 20i_1 - 8i_2 = 0 \dots\dots\dots (2)$$

Solving equation (1) & (2)

$$i_1 = -12 \text{ A}$$

$$i_2 = 4 \text{ A}$$

From i_1 & i_2 , we can find voltage,

$$V_{ab} = 8i_2 = 32 \text{ V}$$

$$V_{65} = 16 \times (i_2 - i_1) = 256 \text{ V}$$

$$V_{64} = 4 \times (i_1 - i_2) = -64 \text{ V}$$

Answer to the question of post lab report 02:

The theoretical solution of the circuit and solution obtained from PSpice is the same.

Conclusion:

We have learnt about dependent sources and theoretically calculated all the currents and voltages and found no discrepancy in PSpice.

