



Department of Computer Science and Engineering

Course Title: Electrical Circuits

Course Number: 209

Semester: 4th

Experiment No.: 06

Experiment Title: Verification of Thevenin's theorem.

Student ID: 2020-3-60-012

Student Name: Sadia Islam Prova

Date of Performance: 23-12-21

Date of Report Submission: 07-01-22

Objectives:

To verify Thevenin's theorem theoretically, experimentally and using PSpice simulation.

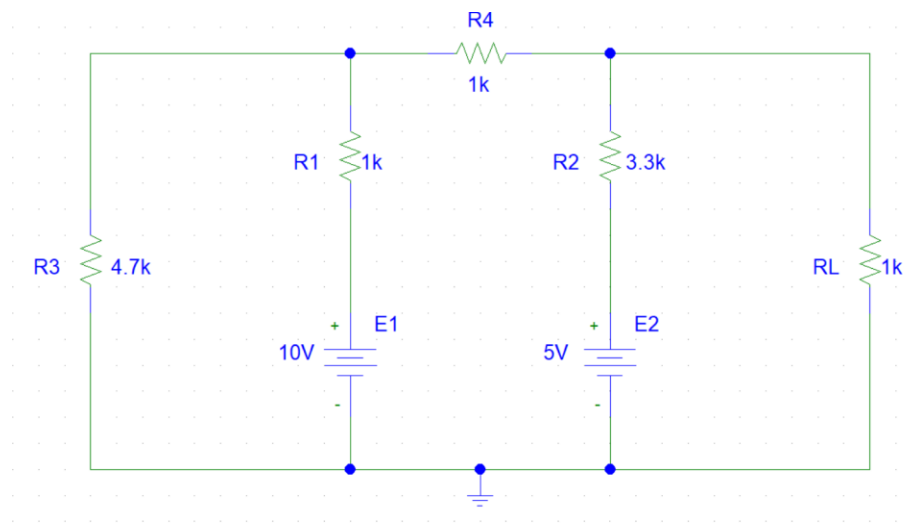
Circuit Diagram:

Figure - 1: Circuit whose Thevenin's equivalent to be determined

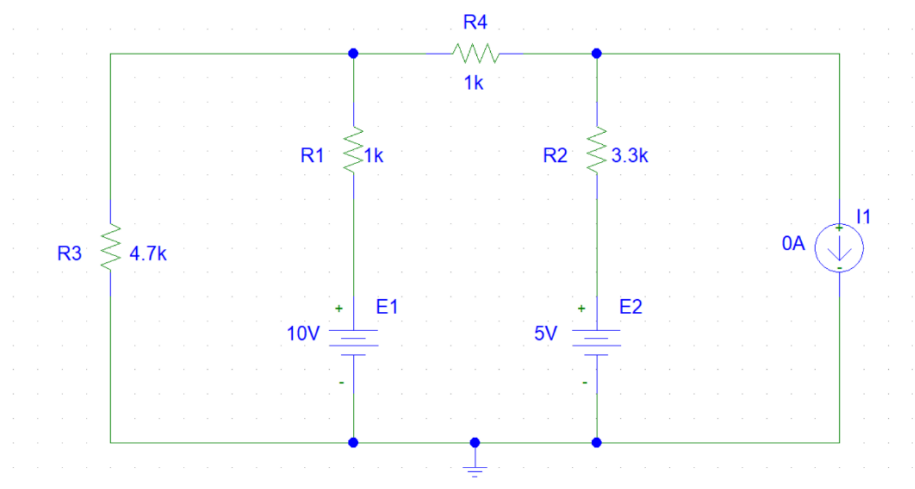


Figure - 2: Circuit to measure the open-circuit voltage

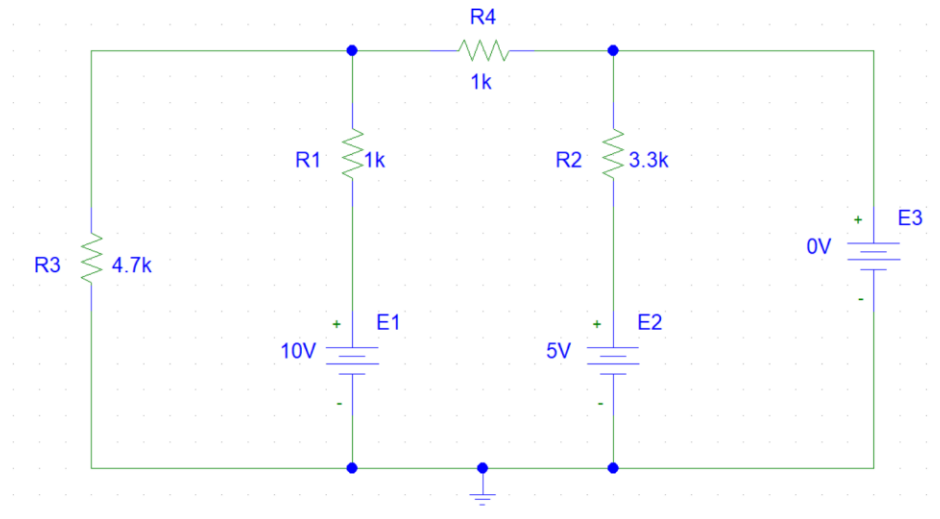


Figure - 3: Circuit to measure the short-circuit current.

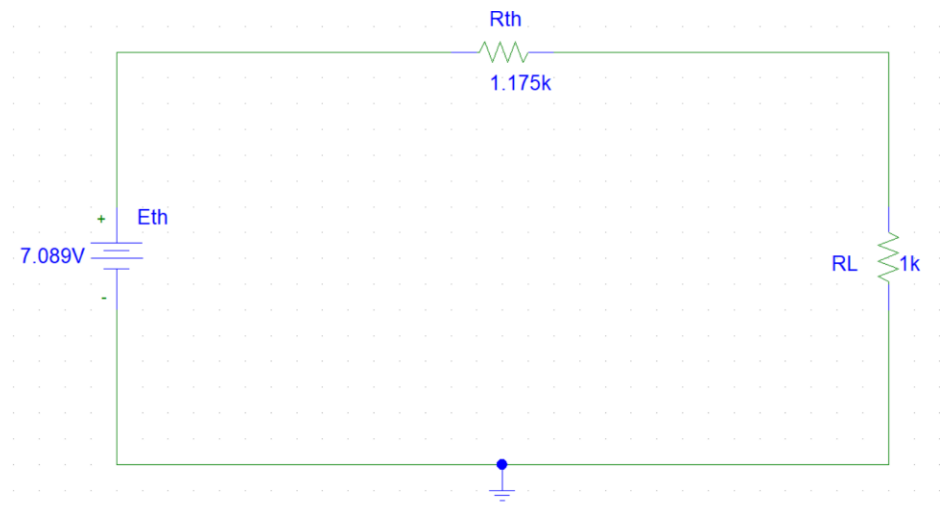


Figure - 4: Circuit to verify Thevenin's theorem

Table 01. Experimental-datasheet for determining Thevenin's equivalent circuit

Measured Value of E_1 (V)	Measured Value of E_2 (V)	Measured Value of V_L (V)	Measured Value of I_L (mA)	Measured Value of V_{oc} (V)	Measured Value of I_{sc} (mA)	Measured Values of Resistors (k)
10	5	3.260	3.260	7.090	6.034	$R_1 = 1, R_2 = 3.3, R_3 = 4.7, R_4 = 1, R_L = 1$

Table 02. Experimental-datasheet for Thevenin's equivalent circuit

$V_{oc} = E_{Th}$ (V)	$R_{Th} = V_{oc} / I_{sc}$ (k-ohm)	Measured Value of V_L (V)	Measured Value of I_L (mA)
7.090	1.175	3.259	3.259

Answer to the question of post lab report 01:

From figure - 1:

Applying KVL on

mesh - 1,

$$4.7i_1 + i_1 - i_2$$

$$+ 10 = 0$$

$$5.7i_1 - i_2 = -10 \dots \dots (1)$$

Applying KVL on mesh - 2,

$$-10 + i_2 - i_1 + i_2 + 3.3i_2 - 3.3i_3 - 5 = 0$$

$$-i_1 + 5.3i_2 - 3.3i_3 = 5 \dots \dots (2)$$

Applying KVL on mesh - 3,

$$-5 + 3.3i_3 - 3.3i_2 + i_3 = 0$$

$$-3.3i_2 + 4.3i_3 = 5 \dots \dots (3)$$

Solving (1), (2) & (3) -

$$i_1 = 1.27 \text{ mA}$$

$$i_2 = 2.733 \text{ mA}$$

$$i_3 = 3.260 \text{ mA} = I_L$$

$$\text{So, } V_L = I_L R_L = (3.260 \times 1) \text{ V} = 3.260 \text{ V}$$

From figure - 2:

Applying KVL on
 mesh - 1,
 $4.7i_1 + i_1 -$
 $i_2 = -10$
 $5.7i_1 - i_2 = -10 \dots \dots (1)$

Applying KVL on mesh - 2,
 $-10 + i_2 - i_1 + i_2 + 3.3i_2 = -5$
 $-i_1 + 5.3i_2 = 5 \dots \dots (2)$

Solving (1) & (2) –

$$i_1 = -1.643 \text{ mA}$$

$$i_2 = 0.633 \text{ mA}$$

$$\text{So, } V_{OC} = (3.3 \times 0.633) + 5 = 7.089 \text{ V} = E_{th}$$

From figure - 3:

Applying KVL on
 mesh - 1,
 $4.7i_1 + i_1 -$
 $i_2 = -10$
 $5.7i_1 - i_2 = -10 \dots \dots (1)$

Applying KVL on mesh - 2,
 $-i_1 + 5.3i_2 - 3.3i_3 = 5 \dots \dots (2)$

Applying KVL on mesh - 3,
 $- 3.3i_2 + 3.3i_3 = 5 \dots \dots (3)$

Solving (1), (2) & (3) -
 $i_1 = - 0.962 \text{ mA}$
 $i_2 = 4.519 \text{ mA}$
 $i_3 = 6.034 \text{ mA} = \text{ISC}$

So, $R_{Th} = V_{OC} / I_{SC} = (7.089 / 6.034) \text{ ohm} = 1.175 \text{ k-ohm}$

From figure - 4:

$I_L = V_{OC} / (R_{Th} + R_L)$
 $= 7.089 / (1.175 + 1)$
 $= 3.259 \text{ mA}$
 $V_L = I_L R_L = 3.259 \times 1 = 3.259 \text{ V}$

So, the Thevenin's theorem verified.

Answer to the question of post lab report 02:

The theoretical solution of the circuit and solution obtained from PSpice is the same.

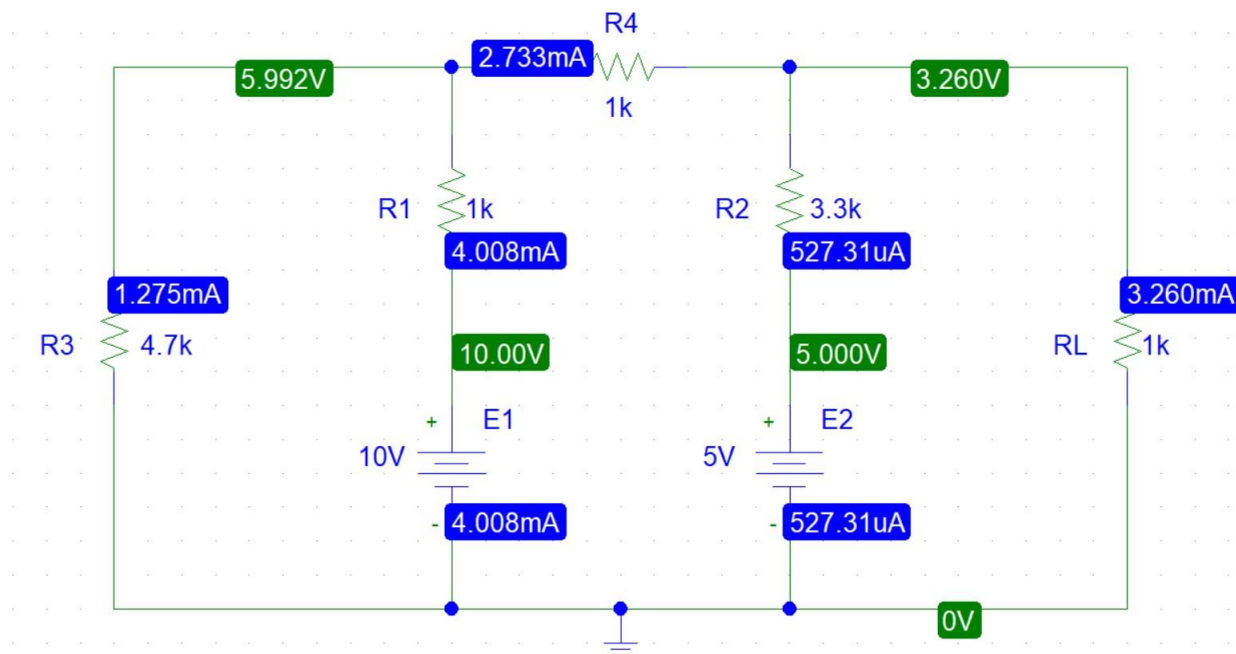
Answer to the question of post lab report 03:

Figure - 5: Circuit whose Thevenin's equivalent to be determined

From figure - 5,

$$V_L = 3.260 \text{ V}$$

$$I_L = 3.260 \text{ mA}$$

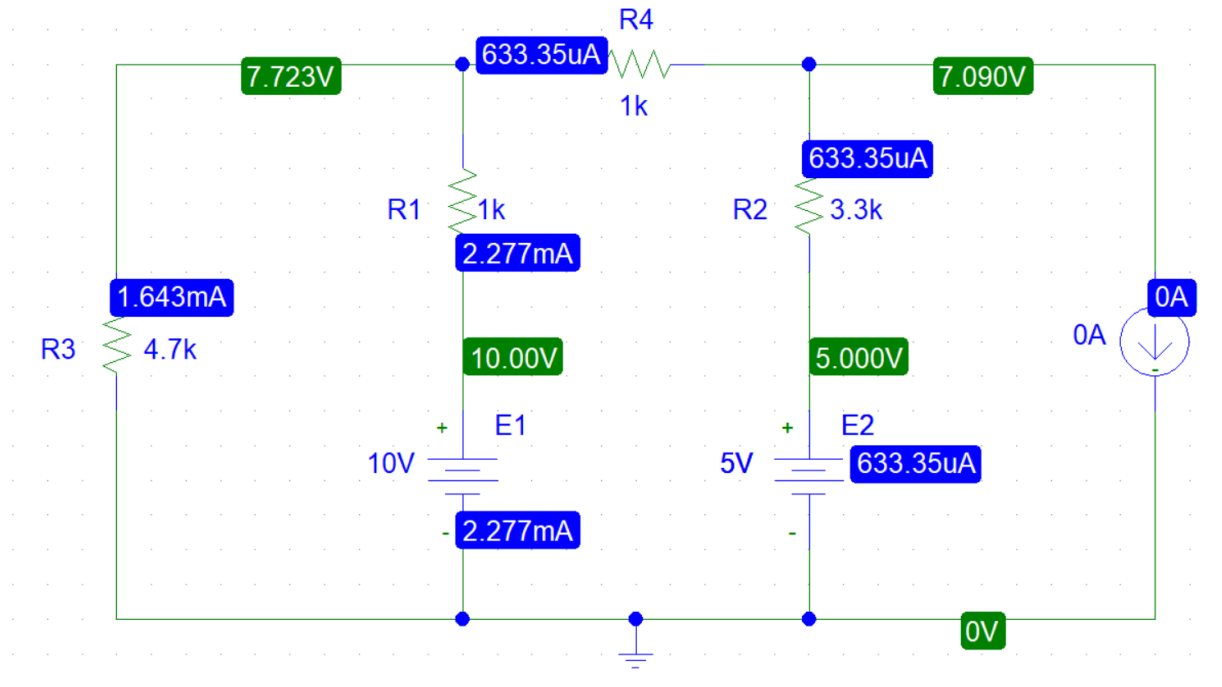


Figure - 6: Circuit to measure the open-circuit voltage

From figure - 6,

$$V_{OC} = 7.090 \text{ V}$$

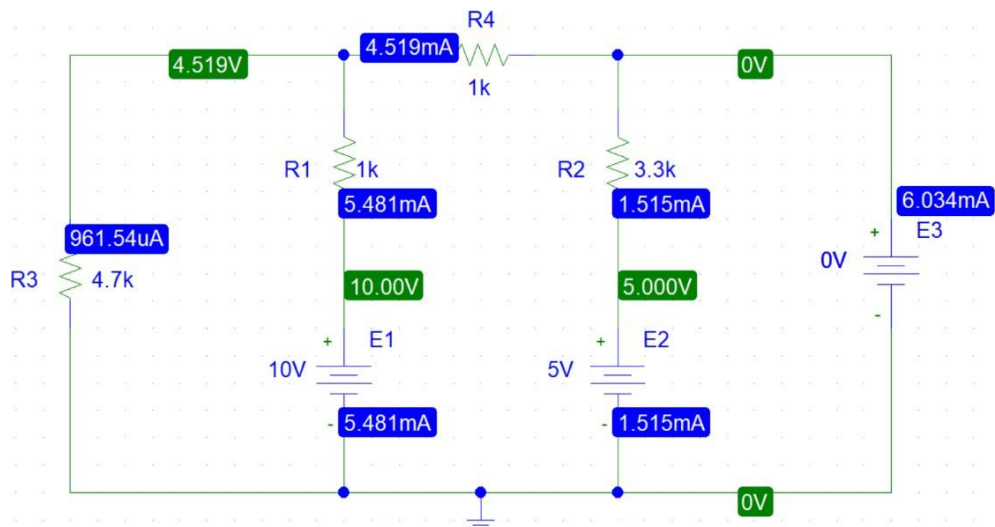


Figure - 7: Circuit to measure the short-circuit current

From figure - 7,

$$I_{SC} = 6.034 \text{ mA}$$

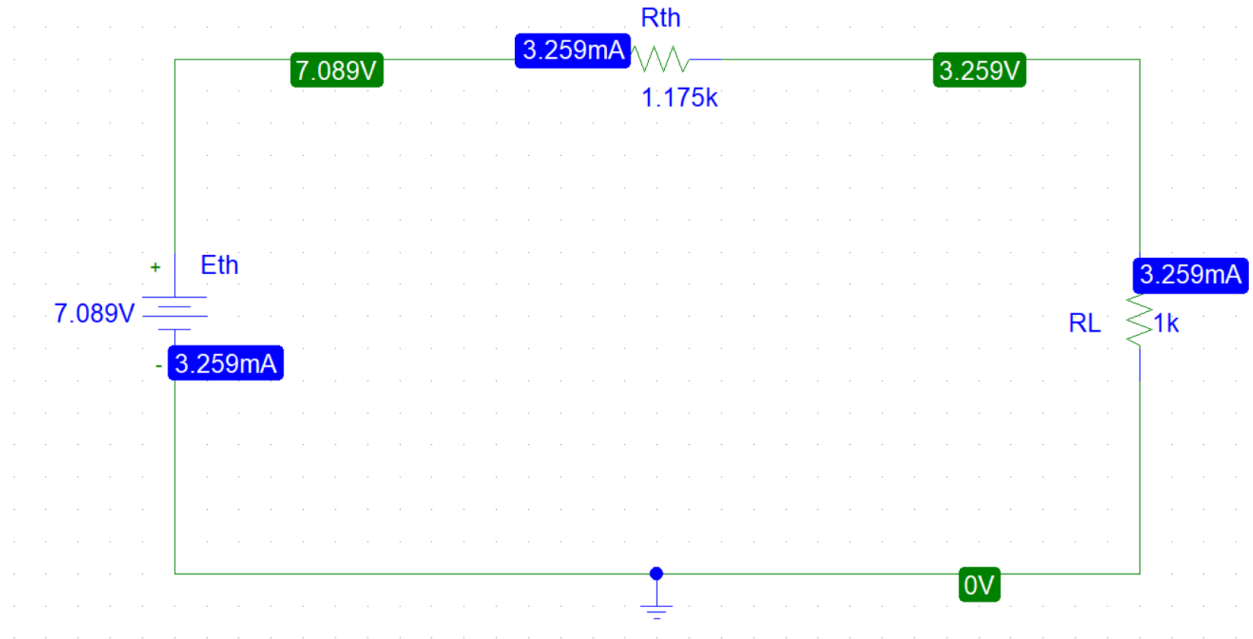


Figure - 8: Circuit to verify Thevenin' theorem.

From figure - 8,

$$V_L = 3.259 \text{ V}$$

$$I_L = 3.259 \text{ mA}$$

Conclusion:

In this experiment, we learn the verification of Thevenin's theorem. Then, compared the theoretical values with experimental values & found frictional discrepancy.

