



EAST WEST UNIVERSITY

Department of Computer Science and Engineering

Course Title: Electrical Circuits

Course Number: 209

Semester: 4th

Project Title: PSpice Analysis for Maximum Power Transfer

Submitted By:

Student ID: 2020-3-60-012

Student Name: Sadia Islam Prova

Date of Performance: 08-01-2022

Date of Report Submission: 09-01-2022

Submitted To:

Rashedul Amin Tuhin

Senior Lecturer

Department of Computer Science & Engineering

Answer to the Question no:01

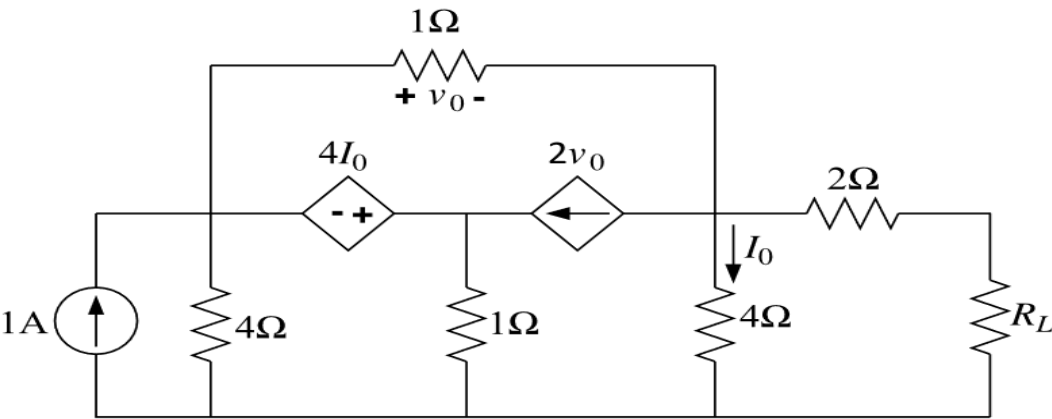


Figure 01: The original circuit given in the question

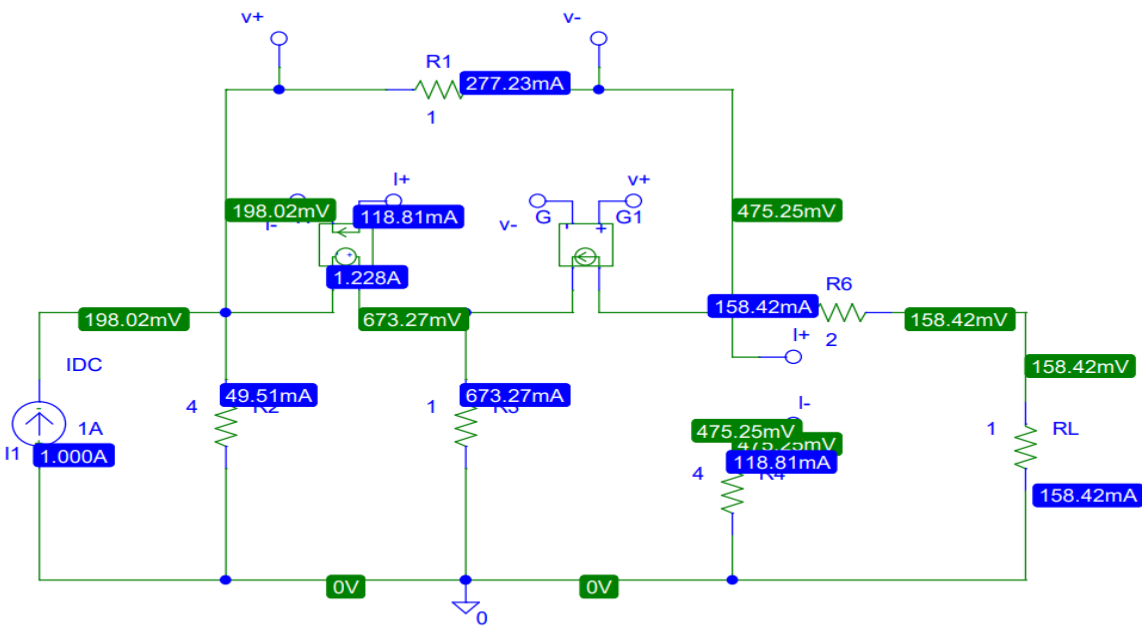


Figure 02: Simulated circuit from figure 1

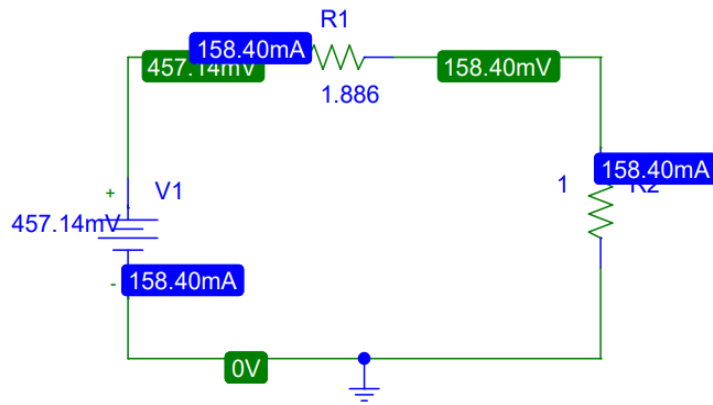


Figure 05: Thevenin's equivalent circuit

Answer to the Question no:02

From figure 01,

Applying KVL at SM , $4i_3 + i_2 + 4i_3 - i_3 - i_0 - i_3 = 2i_2$(i)

Applying KCL at node x, $i_2 - i_3 = 2i_2$ (ii)

Applying KVL at mesh 1, $4 - 4i_1 - 4i_3 - i_1 + i_3 = 0$ (iii)

Solving equation (i),(ii),(iii);

$$V_{Th} = 4I_o = 0.45714V = 457.14mV$$

Again,from figure 01,

Applying KVL at SM , $4(i3 - i4) + i1 + 4(i3 - i4)i3 - i2 = 0$(i)

Applying KCL at node Y, $i1 - i3 = 2i1$ (ii)

Applying KVL at mesh 2, $-4i2 + 4(i3 - i4) - i2 + i3 = 0$ (iii)

Applying KVL at mesh 4, $4(i4 - i3) + 2i4 + 1 = 0$ (iv)

Solving equation (i),(ii),(iii),(iv); $R_{th} = R_L = 1.88571 \text{ ohm}$

$P_{max} = (V_{Th})^2 / 4 R_{th} = 0.0277 \text{ W} = 27.7 \text{ mW}$

Answer to the Question no:03

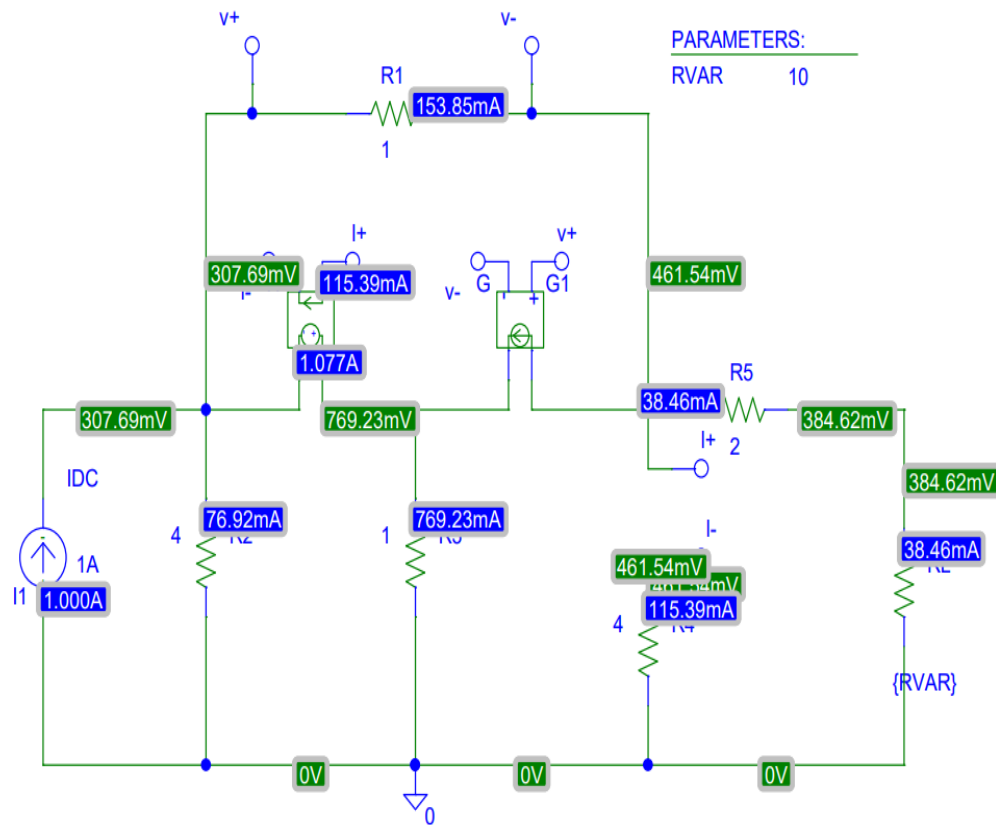


Figure 06: Maximum power circuit



Figure 07: RL VS Pmax graph

Answer to the Question no:04

Table 1. Comparison of R_L and maximum power:

	Step 2	Step 3
R_L	1.89 ohm	1.89 ohm
P_{\max}	0.00277 W	27.706mW = 0.0277W

There is no discrepancy in the value of R_L and maximum power obtained in step 2 and 3.

